

To: Professor Darish
From: Trevor Wagenhals
Subject: Power Analysis in AC
Circuits

Date: 4/07/2015
Course & Section Number:
Partner(s):
TA:

SUMMARY

EXPERIMENTAL APPROACH


Equipment and Materials

- Oscilloscope
- Function Generator
- Protoboard
- Inductors, resistors, and capacitors
- Banana clips, BNC cables, probes
- Power supply

Procedure

This experiment involved calculating complex power through different measurements. Calculating voltage drop and current across a resistor allowed the active power to be calculated at each resistor. Taking the conjugate of the current and the effective current, the reactive power could then be calculated across each inductor and capacitor. Adding the active powers and reactive powers up and combining them will give the complex power S , throughout the circuit.

DISCUSSION OF RESULTS

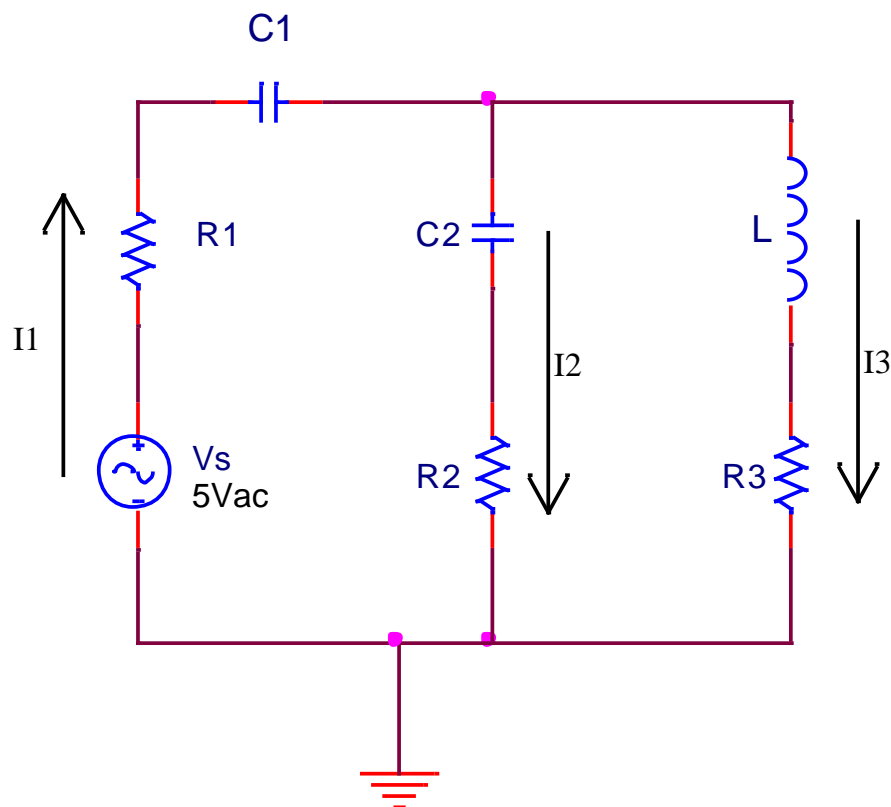

Calculating I_2 and I_3 equivalent by either nodal analysis or simply combining the parallel circuit, I_1 can be calculated. Once I_1 is calculated I_2 and I_3 can then be calculated by just doing current division across each branch. Once all there currents were calculated, the voltage drop across each material could be calculated by ohms laws. Power at each material can finally be calculated by the complex power rules.

Table 6.1.

	Calculations			Measurements		
	Phasor		RMS- value	Phasor		RMS- value
	Rectangular	Polar		Rectangular	Polar	
I_1	$.20478 - j.13674 \text{ A}$	$.246 \angle -33.73^\circ \text{ A}$	$.174 \angle -33.73^\circ \text{ A}$	$.206 - j.13596 \text{ A}$	$.246822 \angle -33.42^\circ \text{ A}$	$.1744 \angle -33.42^\circ \text{ A}$
I_2	$.178 - j.0920$	$.2006 \angle 27.31^\circ \text{ A}$	$.141 \angle 27.31^\circ \text{ A}$	<i>No data are needed in this cell</i>		
I_3	$.0343 - j.8485$	$.8492 \angle -87.68^\circ \text{ A}$	$.600 \angle -87.68^\circ \text{ A}$			

After the currents have been calculated, plugging them into the equations below allow for the active and reactive powers to be calculated. In order to ensure that the procedure was done properly, the equation for the source power and the equation for the summation of the power should cancel out to equal 0. When comparing the results, there was minimal error to conclude that the data was accurate.

The error in data can easily be complimented to the internal impedance and resistance of the equipment used to take all the measurements.

Table 6.2.

		Calculations		Measurements	
		Active	Reactive	Active	Reactive
Power generated by source	$\dot{S}_{source} = \frac{1}{2} \dot{V}_S \cdot \hat{I}_1$, mVA	511.95 mW	-j341.85 mVAR	515.05	-j339.9
Active power consumed by circuit	$I_{1, eff}^2 \cdot R_1$, mW	171 mW		168.9 mW	
	$I_{2, eff}^2 \cdot R_2$, mW	238 mW		244.04 mW	
	$I_{3, eff}^2 \cdot R_3$, mW	117.6 mW		103.67 mW	
	$\sum I_{n, eff}^2 \cdot R_n$, mW	526.6 mW		516.61 mW	
Reactive power consumed by circuit	$I_{3, eff}^2 \cdot X_L$, mVAR.....	173 mVAR		169.7 mVAR	
	$I_{1, eff}^2 \cdot X_{C1}$, mVAR.....	-505 mVAR		-502 mVAR	
	$I_{2, eff}^2 \cdot X_{C2}$, mVAR.....	-8.38 mVAR		-9.8 mVAR	
	$\sum I_{n, eff}^2 \cdot X_n$, mVAR	-340.38 mVAR		-342.1 mVAR	

Questions

4.1. Why don't we need to get additional information about the phase of the branch currents for evaluating the power in the discrete components? (By using Fluke meter we are measuring only the effective (RMS) values of currents in those components.)

The phase of the current is not needed in the calculation of the reactive or the active power, so by just determining the effective current, both powers can be calculated, regardless of the phase that the current is at.

4.2. Explain the physical meaning of the principle of conservation of power in AC-circuits.

Because power cannot be created nor destroyed, just like the components that make it up, then if the individual powers of components that make up a circuit are found, then the complex power is simply the combination of all of the powers.