

ECE 312 Experiment 1: BJT Small Signal Parameters (7/13/2017)
Trever Wagenhals

SUMMARY

This lab is an introduction to the use of LabView to determine the four parameters forming the hybrid or h parameter small signal model of a CA3046 bipolar transistor array. With the h parameter discovered, the hybrid π small signal parameters can be determined at particular frequencies. Upon completion, three out of four of our parameters were successfully verified with error remaining in one calculation.

Procedure

The first task was to use circuit analysis on Figure 1.1 to determine the theoretical values. As the summary stated, the goal is to determine the h parameters of the BJT. In order to execute the small signal analysis, these results are dependent on DC analysis results first, such as I_c , I_b , and I_e . So, typically to perform small signal analysis we must do DC analysis first. However, because I_c and V_{ce} were provided for us, the DC analysis is not necessary in order to find out all four parameters.

V_{ce} is given to us, but V_{ce} can also be calculated and verified by knowing the following equation:

$$V_{ce} = 6 - R_{c1}I_c + 300I_c \rightarrow V_{ce} = 6 - 2.7k(1mA) + 300(1mA) \rightarrow V_{ce} = 3$$

Now, we can start by calculating h_{fe} . By knowing:

$$h_{fe} = \frac{i_c}{i_b}, \quad I_b = \frac{I_c}{\beta}, \quad I_c = 1mA$$

and also knowing through the TA the beta value to be used for the CA3046 is $\beta \sim 250$,

$$I_b = \frac{1mA}{250} \rightarrow 4\mu A$$

$$H_{fe} = 1mA/4\mu A \rightarrow H_{fe} = 250 \text{ (It turns out our } H_{fe} \text{ will be equal to our } \beta \text{ in this problem)}$$

Next, we can calculate H_{ie} by knowing that V_{be} is typically around 0.7V. Thus:

$$H_{ie} = V_{be} / I_b \rightarrow H_{ie} = 0.7V / 4\mu A \rightarrow H_{ie} = 175k\Omega$$

With V_{ce} given and verified as 3V and V_{be} estimated, we can solve for H_{re} :

$$H_{re} = V_{be} / V_{ce} \rightarrow H_{re} = 0.7 / 3 \rightarrow H_{re} = 0.233$$

Lastly, H_{oe} can be solved:

$$H_{oe} = I_c / V_{ce} \rightarrow H_{oe} = 1mA / 3V \rightarrow H_{oe} = 1.43 * 10^{-3}$$

Observations and Discussion

The actual results varied from the calculated results quite a bit. With our circuit designed so that I_c would hopefully be 1mA and V_{ce} 3V, these numbers were actually slightly different. I decided to read the specifications sheet more to determine why these variances were so large. When I looked, the β value that was provided to us was much larger than the typical 40-100 seen by the transistor operating at $I_c = 1mA$. Without redoing all of these calculations in detail, it can be seen that By changing β , I_b would be higher at 10 μA . This would change the value of h_{fe} to 100 instead of 250. This is much closer to the typical value of 110 shown in the spec sheet.

By changing I_b to a higher 10uA, H_{ie} ultimately ends up changing value as well. V_{be} also varied slightly from the initial expected 0.7. The spec sheet says that in these conditions, it should be closer to 0.715. This slight variance will cause H_{ie} to be slightly different at 0.715/10uA. Now, the new calculation would be 71.5kΩ.

As stated in the lab, we had to use Figure 1.2 to calculate H_{oe} and H_{re} properly. This circuit changes the values for the initially stated I_c and V_{ce} , resulting in major changes in the calculations. Now, V_{ce} is 1V instead of 3V and I_c can be recalculated using:

$$V_{cc} = R_{c}I_c + V_{ce} + I_e R_e \rightarrow I_e \sim I_c \rightarrow V_{cc} = R_{c}I_c + V_{ce} + I_c R_e \rightarrow I_c = \frac{V_{cc} - V_{ce}}{R_c + R_e} \rightarrow I_c = 1.6\text{mA}$$

$$H_{re} = \frac{V_{be}}{V_{ce}} \rightarrow H_{re} = \frac{V_{be}}{1} \rightarrow H_{re} = V_{be}$$

$$H_{oe} = \frac{I_c}{V_{be}} \rightarrow H_{oe} = 1.6\text{mA} / V_{be}$$

So, even with these adjusted calculations, it can be seen that the only parameter that was fixed by using the spec sheet was H_{fe} . The H_{ie} was still much higher than the spec sheet indicated and H_{re} and H_{oe} are dependent on a value of V_{be} that is not mentioned in the spec sheet. As mentioned in the beginning, DC analysis can be performed to determine this value, but even with a new V_{be} , unless it were to equate to 102V, which is completely unrealistic, these parameters would never line up with the values in the spec sheet. This leads me to believe that somehow my calculations were messed up, but at this point I do not see where the issue lies.

When the circuit was evaluated instead of just calculated, the results were actually much more in line with the spec sheet.

To determine H_{ie} in the circuit, V_s was set so that $V_{ce} = 0$. This value was 15mV, which resulted in V_{be} to be about 10mV. Because $V_{ce} = 0$, we cannot use the equation we used to initially calculate H_{ie} ; but, now we can use the equation $h_{ie} = \frac{R_s}{\frac{V_s}{V_{BE}} - 1} \rightarrow H_{ie} = 5.3\text{k}\Omega$. This value is much closer to the expected 3.5kΩ than the calculated value.

Measuring I_c to be about 0.180mA, H_{fe} can now be recalculated and is approximately 103. Once again, this is close to the spec sheet and our one result that actually calculated correctly.

By creating the circuit in Figure 1.2, the unknown value for V_{be} can be determined as 100mV. I_c was also much lower than what was calculated at 2.4uA. Now, when calculated H_{oe} is 24uS, which is close to the expected 15.6uS.

The last parameter, H_{re} equates to V_{be} , which was said to be 100mV, so it is 0.1. This does not match the data sheet of 1.8×10^{-4} . My calculation from the original circuit, from the spec sheet, and from the design did not meet the expected value.

Conclusion

My initial estimates based on the given values for V_{ce} and I_c did not lead to the correct parameter values. My recalculation using the spec sheet fixed one of the parameters, but three of them still did not align. In my actual design, ¾ of the parameters were within reason. The one that was not correct for my design was also wrong in calculation, which leads me to believe that I was doing my calculations wrong for this parameter. Overall, the circuit functioned as expected with one parameter not fully understood.

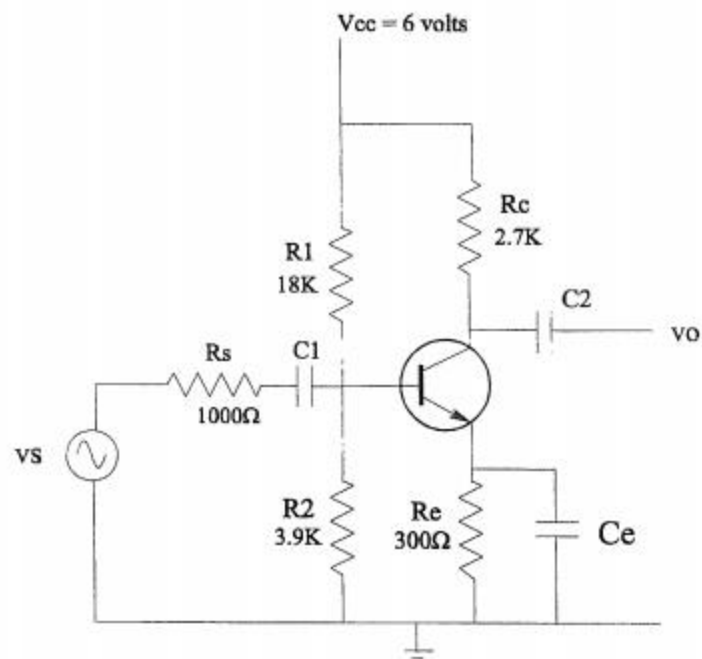


Figure 1.1 Single stage CE BJT amplifier

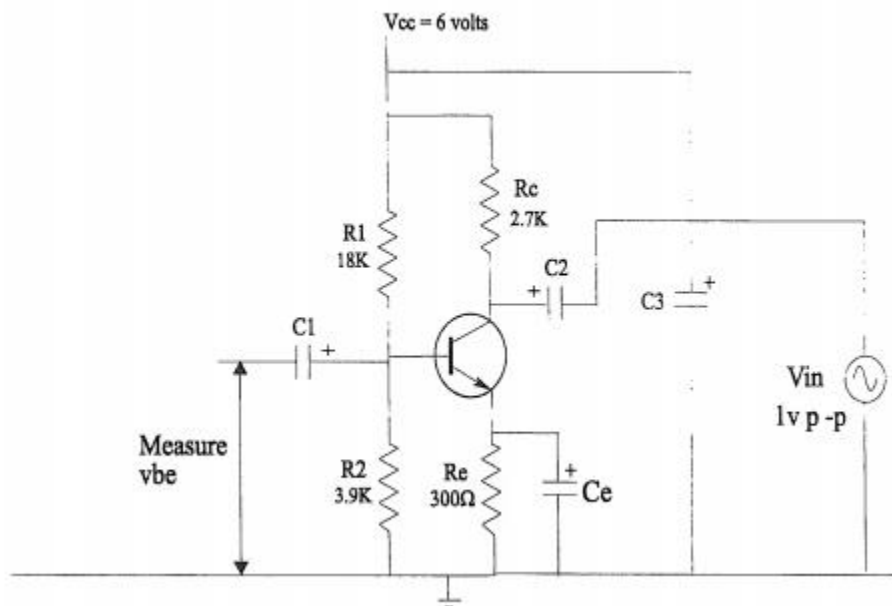


Figure 1.2 Modification for the measurement of H_{re} and H_{ie}